

ITP PHYSICAL COMPUTING


Using a transistor to control high current loads with an Arduino

In this tutorial, you'll learn how to control a high-current DC load such as a DC motor or an incandescent light from a microcontroller.


(:toc Table of Contents:)

Parts

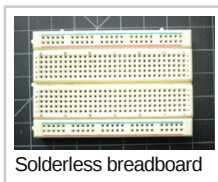You will need the following parts for this tutorial.



Solderless breadboard

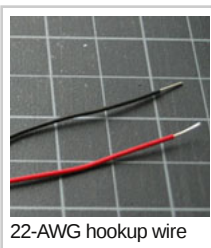


22-AWG hookup wire



Arduino Microcontroller module




10Kohm potentiometer

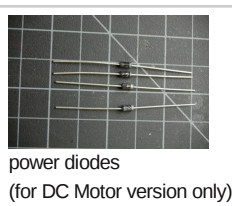

power diodes
(for DC Motor version only)




DC power supply

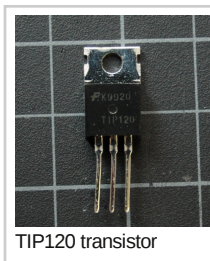

TIP120 transistor


- or -

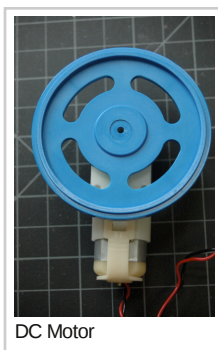

DC Motor




Incandescent lamp and socket

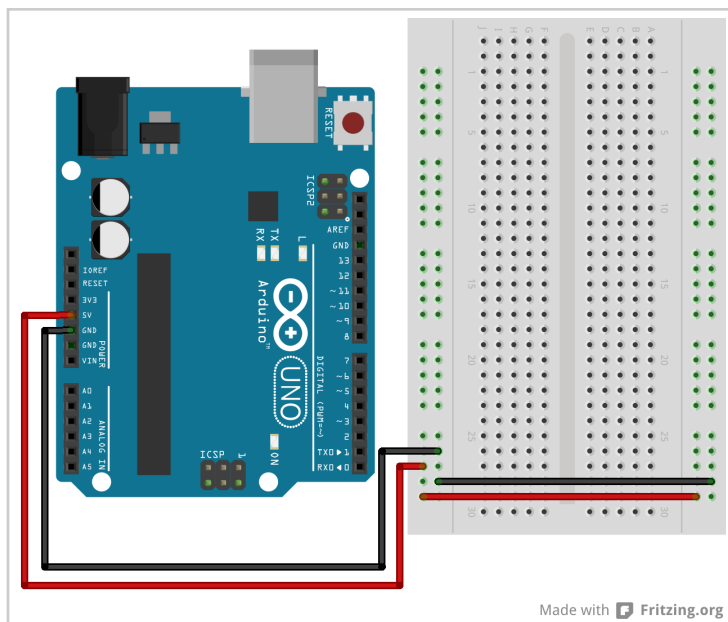


(Diagram made with [Fritzing](#))

Add a potentiometer

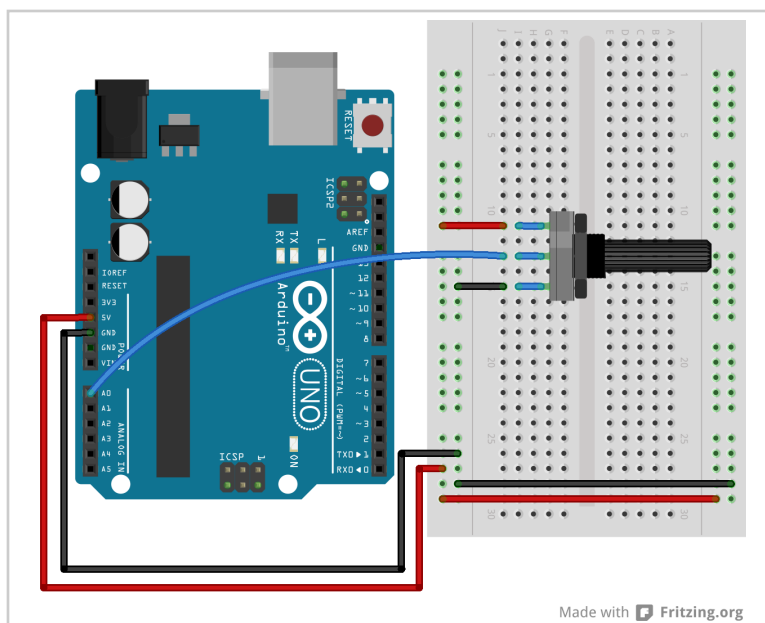Connect a potentiometer to analog in pin 0 of the module:




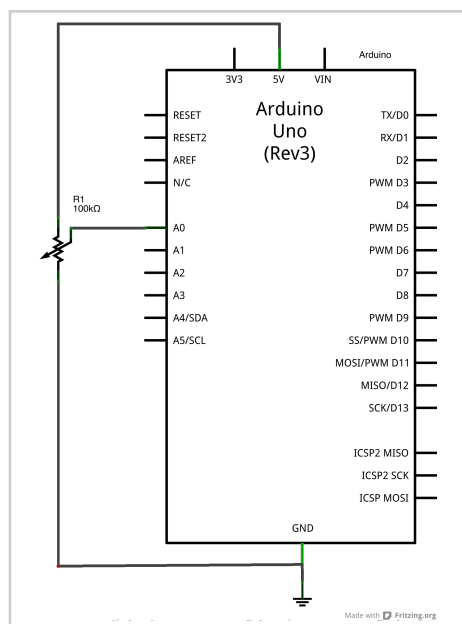

(Diagram made with [Fritzing](#))


Connect a transistor to the microcontroller

The transistor allows you to control a circuit that's carrying higher current and voltage from the microcontroller. It acts as an electronic switch. The one you're using for this lab is an NPN-type transistor called a TIP120. The datasheet for it can be found [here](#). It's designed for switching high-current loads. It has three connections, the base, the collector, and the emitter. The base is connected to the microcontroller's output. The high-current load (i.e. the motor or light) is attached to its power source, and then to the collector of the transistor. The emitter of the transistor is connected to ground.

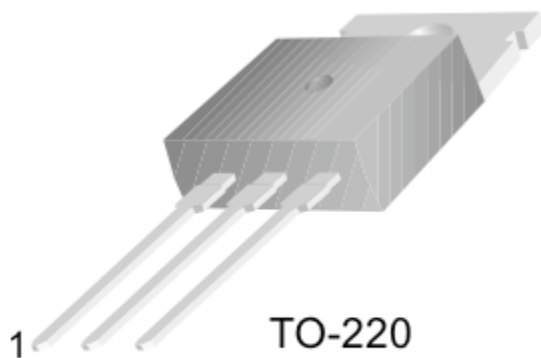

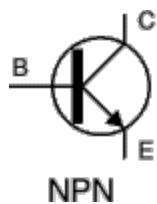1.Base 2.Collector 3.Emitter


Pinout of a TIP-120 transistor, from left to right: base, collector, emitter.



Note: you can also use an IRF510 or IRF520 MOSFET transistor for this. They have the same pin configuration as the TIP120, and perform similarly. They can handle more amperage and voltage, but are more sensitive to static electricity damage.


The schematic symbol of an NPN transistor where B is the base, C is the collector, and E is the emitter.

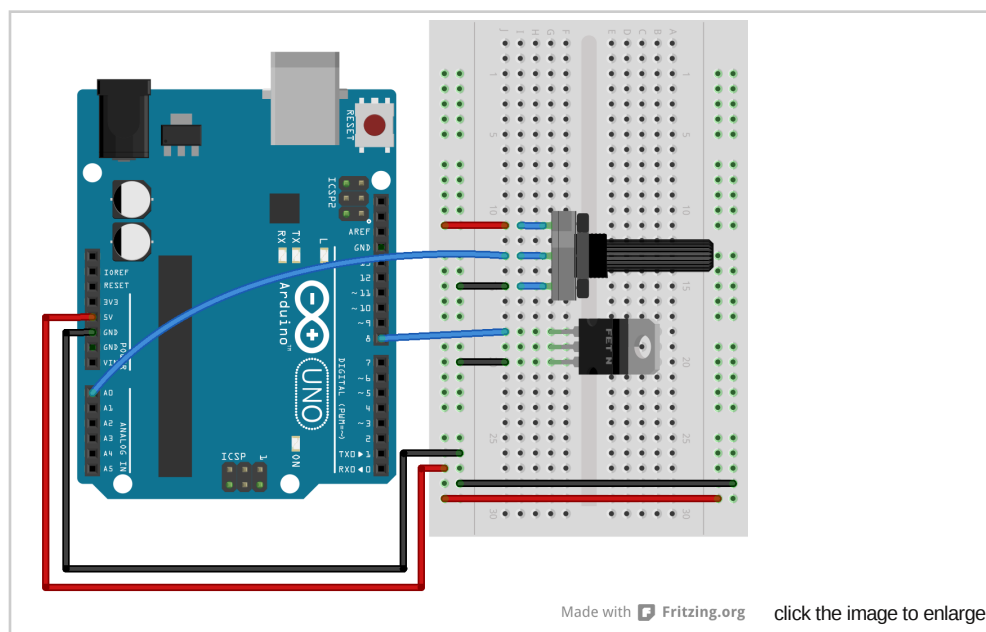Connect the base to an output pin of the microcontroller, and the emitter to ground like so:





Connect a motor and power supply

Attach a DC motor to the collector of the transistor. Most motors will require more amperage than the microcontroller can supply, so you will need to add a separate power supply as well. If your motor runs on around 9V, you could use a 9V battery. A 5V motor might run on 4 AA batteries. a 12V battery may need a 12V wall wart, or a 12V battery. The ground of the motor power supply should connect to the ground of the microcontroller, on the breadboard.

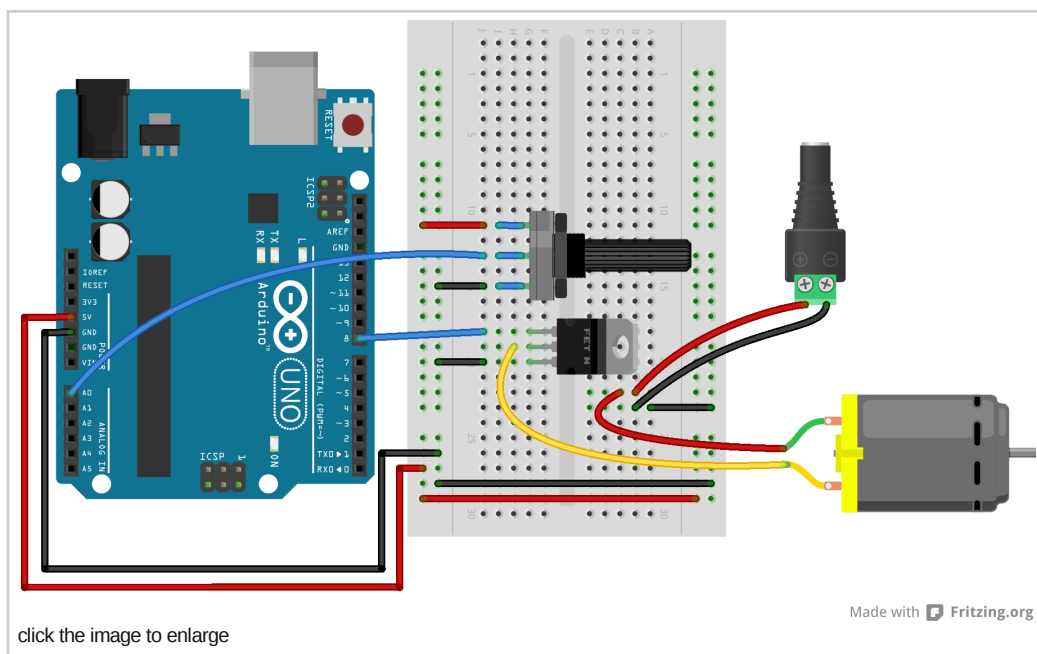


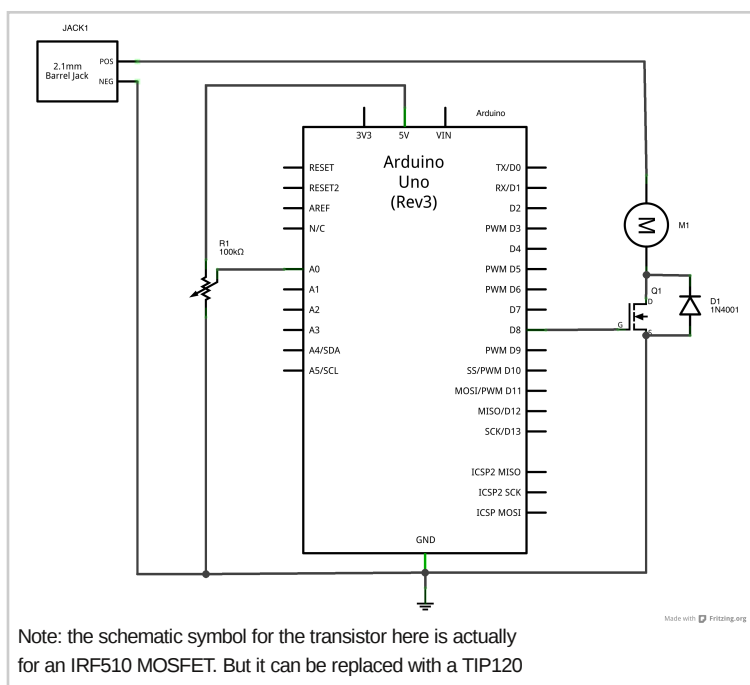Finally, add diode in parallel with the collector and emitter of the transistor, pointing away from ground. The diode protects the transistor from back voltage generated when the motor shuts off, or if the motor is turned in the reverse direction.



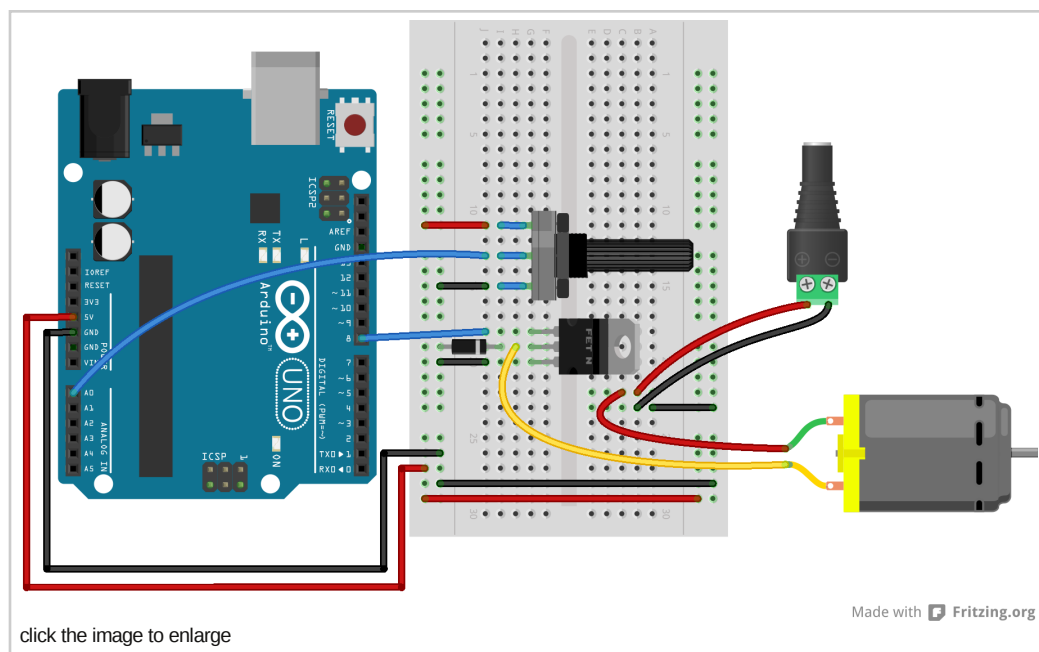

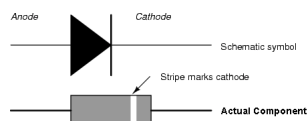Be sure to add the diode to your circuit correctly. The silver band on the diode denotes the cathode which is the tip of the arrow in the schematic, like so:





click the image to enlarge

This circuit assumes you're using a 12V motor. If your motor requires a different voltage, make sure to use a power supply that's appropriate. Connect the ground of the motor's supply to the ground of your microcontroller circuit, though, or the circuit won't work properly.

Connect a lamp instead

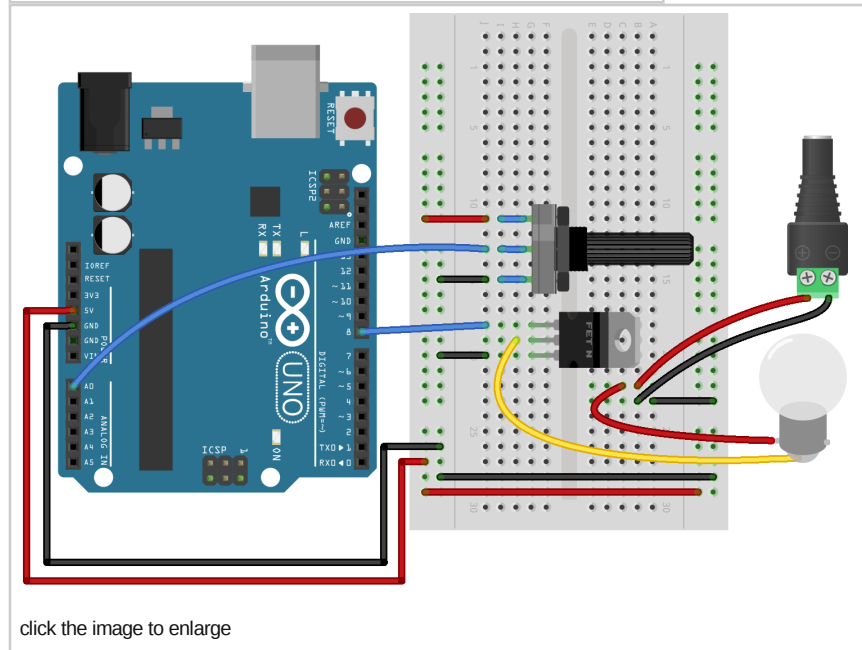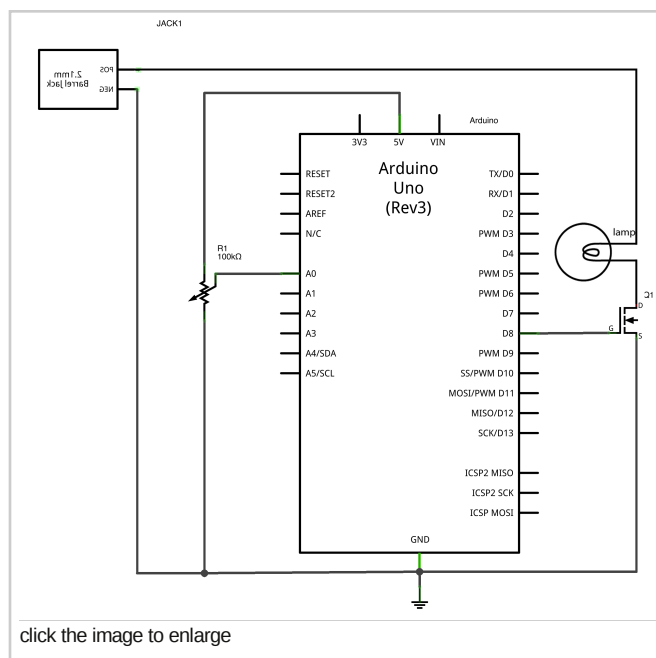You could also attach a lamp using a transistor. Like the motor, the lamp circuit below assumes a 12V lamp. Change your power supply accordingly if you're using a different lamp. In the lamp circuit, the protection diode is not needed, since there's no way for the polarity to get reversed in this circuit:



Program the microcontroller

Write a quick program to test the circuit. Your program should make the transistor pin an output in the setup method. Then in the loop, it should turn the motor on and off every second, just like the [blink sketch](#) does.

Now that you see it working, try changing the speed of the motor or the intensity of the lamp using the potentiometer.

To do that, read the voltage of the potentiometer using `analogRead()`. Then map the result to a range from 0 to 255 and save it in a new variable. Use that variable to set the speed of the motor or the brightness of the lamp using `analogWrite()`.

Notes

For the motor users:

A motor controlled like this can only be turned in one direction. To be able to reverse the direction of the motor, an H-bridge circuit is required. For more on controlling DC motors with H-bridges, see the [DC Motor Control lab](#)

Page last modified on September 21, 2013, at 08:45 AM