

[Courseware \(/courses/UTAustinX/UT.6.01x/1T2014/courseware\)](/courses/UTAustinX/UT.6.01x/1T2014/courseware)[Course Info \(/courses/UTAustinX/UT.6.01x/1T2014/info\)](/courses/UTAustinX/UT.6.01x/1T2014/info)[Discussion \(/courses/UTAustinX/UT.6.01x/1T2014/discussion/forum\)](/courses/UTAustinX/UT.6.01x/1T2014/discussion/forum)[Progress \(/courses/UTAustinX/UT.6.01x/1T2014/progress\)](/courses/UTAustinX/UT.6.01x/1T2014/progress)[Questions \(/courses/UTAustinX/UT.6.01x/1T2014/a3da417940af4ec49a9c02b3eae3460b/\)](/courses/UTAustinX/UT.6.01x/1T2014/a3da417940af4ec49a9c02b3eae3460b/)[Syllabus \(/courses/UTAustinX/UT.6.01x/1T2014/a827a8b3cc204927b6efaa49580170d1/\)](/courses/UTAustinX/UT.6.01x/1T2014/a827a8b3cc204927b6efaa49580170d1/)

Normally, the execution speed of a microcontroller is determined by an external crystal. The Stellaris® EK-LM4F120XL and EK-TM4C123GXL boards have a 16 MHz crystal. Most microcontrollers include a phase-lock-loop (PLL) that allows the software to adjust the execution speed of the computer. Typically, the choice of frequency involves the tradeoff between software execution speed and electrical power. In other words, slowing down the bus clock will require less power to operate and generate less heat. Speeding up the bus clock obviously allows for more calculations per second, at the cost of requiring more power to operate and generating more heat.

The default bus speed for the LM4F/TM4C internal oscillator is 16 MHz \pm 1%. The internal oscillator is significantly less precise than the crystal, but it requires less power and does not need an external crystal. The TExaS real-board grader has been turning on the PLL, and in this section we will explain how it work. If we wish to have accurate control of time, we will activate the external crystal (called the main oscillator) use the PLL to select the desired bus speed.

There are two ways to activate the PLL. We could call a library function, or we could access the clock registers directly. In general, using library functions creates a better design because the solution will be more stable (less bugs) and will be more portable (easier to switch microcontrollers). However, the objective of the class is to present microcontroller fundamentals. Showing the direct access does illustrate some concepts of the PLL.

An external crystal is attached to the LM4F/TM4C microcontroller, as shown in Figure 10.1. Table 10.1 shows the clock registers used to define what speed the processor operates. The output of the main oscillator (Main Osc) is a clock at the same frequency as the crystal. By setting the OSCSRC bits to 0, the multiplexer control will select the main oscillator as the clock source.

The main oscillator for the LM4F/TM4C LaunchPad will be 16 MHz. This means the reference clock (Ref Clk) input to the phase/frequency detector will be 16 MHz. For a 16 MHz crystal, we set the XTAL bits to 10101 (see Table 10.1). In this way, a 400 MHz output of the voltage controlled oscillator (VCO) will yield a 16 MHz clock at the other input of the phase/frequency detector. If the 400 MHz clock is too slow, the **up** signal will add to the charge pump, increasing the input to the VCO, leading to an increase in the 400 MHz frequency. If the 400 MHz clock is too fast, **down** signal will subtract from the charge pump, decreasing the input to the VCO, leading to a decrease in the 400 MHz frequency. Because the reference clock is stable, the feedback loop in the PLL will drive the output to a stable 400 MHz frequency.

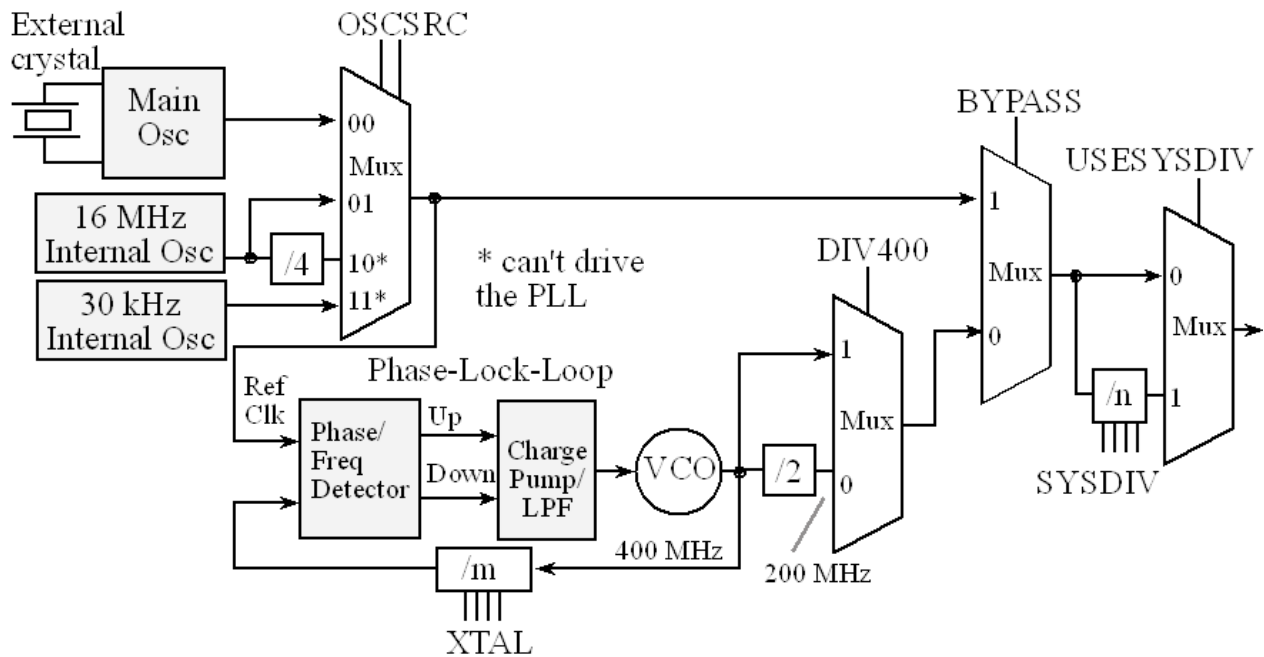


Figure 10.1. Block diagram of the main clock tree on the LM4F/TM4C including the PLL.

XTAL	Crystal Freq (MHz)	XTAL	Crystal Freq (MHz)
0x0	Reserved	0x10	10.0 MHz
0x1	Reserved	0x11	12.0 MHz
0x2	Reserved	0x12	12.288 MHz
0x3	Reserved	0x13	13.56 MHz
0x4	3.579545 MHz	0x14	14.31818 MHz
0x5	3.6864 MHz	0x15	16.0 MHz
0x6	4 MHz	0x16	16.384 MHz
0x7	4.096 MHz	0x17	18.0 MHz
0x8	4.9152 MHz	0x18	20.0 MHz
0x9	5 MHz	0x19	24.0 MHz
0xA	5.12 MHz	0x1A	25.0 MHz
0xB	6 MHz (reset value)	0x1B	Reserved
0xC	6.144 MHz	0x1C	Reserved
0xD	7.3728 MHz	0x1D	Reserved
0xE	8 MHz	0x1E	Reserved
0xF	8.192 MHz	0x1F	Reserved

Address	26-23	22	13	11	10-6	5-4	Name
\$400FE060	SYSDIV	USESYSYDIV	PWRDN	BYPASS	XTAL	OSCSRC	SYSCTL_RCC_R
\$400FE050					PLLIS		SYSCTL_RIS_R
	31	30	28-22	13	11	6-4	
\$400FE070	USERCC2	DIV400	SYSDIV2	PWRDN2	BYPASS2	OSCSRC2	SYSCTL_RCC2_R

Table 10.1. Main clock registers (RCC2 in LM4F/TM4C only).



About (<https://www.edx.org/about-us>) Jobs (<https://www.edx.org/jobs>)
Press (<https://www.edx.org/press>) FAQ (<https://www.edx.org/student-faq>)
Contact (<https://www.edx.org/contact>)



EdX is a non-profit created by founding partners Harvard and MIT whose mission is to bring the best of higher education to students of all ages anywhere in the world, wherever there is Internet access. EdX's free online MOOCs are interactive and subjects include computer science, public health, and artificial intelligence.



(<http://www.meetup.com/edX-Global-Community/>)



(<http://www.facebook.com/EdxOnline>)



(<https://twitter.com/edXOnline>)



(<https://plus.google.com/108235383044095082>)



(<http://youtube.com/user/edxonline>)

© 2014 edX, some rights reserved.

[Terms of Service and Honor Code](#) -
[Privacy Policy \(https://www.edx.org/edx-privacy-policy\)](https://www.edx.org/edx-privacy-policy)